


EE1005 – Digital Logic Design (BCS-2E)
Quiz#3 (CLO-04)

Total Marks: 10

Time Allowed: 10 minutes

Roll #: XXXXXXXXXX

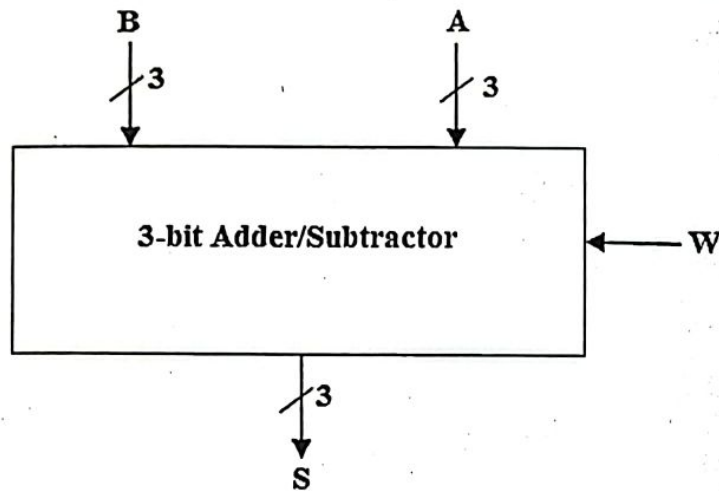Question: A 3-bit adder/subtractor with selection bit W is given below. If $W = 0$, then two 3-bit numbers A and B are added. If $W = 1$, then the two numbers A and B are subtracted. A and B are signed numbers and negative numbers are represented in 2's complement form.



Determine the value of S and OV for the following input values. OV is the overflow flag that is '1' when overflow occurs.

Supposing $A+B$, $A-B$

Inputs			Outputs	
W	A	B	S	OV
0	010	001	✓ 011	0 ✓
0	100 - 4	101 - 3	✓ 001 1011	1 ✓
1	011	111	✓ 100	1 ✓
1	110	111	✓ 111	1 ✓
0	101	001	100	0 ✓

$$\begin{array}{r} 010 \\ + 001 \\ \hline 011 \end{array}$$

$$\begin{array}{r} 1100 \\ + 1101 \\ \hline 11001 \end{array}$$

$$\begin{array}{r} 011 \\ - 111 \\ \hline 0100 \end{array}$$

$$\begin{array}{r} 101 \\ - 001 \\ \hline 100 \end{array}$$

$$\begin{array}{r} 110 \\ - 111 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} 011 \\ + 000 \\ \hline 100 \end{array}$$

Date: April 23, 2024