

## Digital Logic Design

(EE1005)

Date: April 6<sup>TH</sup> 2024

Course Instructor(s)

Ms. Sobia Tariq Javed

Ms. Maimona Akram

Dr. Amjad Hussian

Mr. Amjad Ali

Mr. Aftab Alam

Mr. Zummar Saad

Mr. Salman Shoaib

## Sessional-II Exam

Total Time (Hrs): 1

Total Marks: 50

Total Questions: 3

Roll No

Section


Student Signature

### Instructions:

1. Solve questions 1 and 2 on the answer sheet and solve question 3 on the question paper and attach it with your answer sheet.
2. Show the required steps and label properly to get the full credit.
3. Solve the paper in the sequence provided in the question paper i.e Question 1 should be solved before question 2.

**CLO# 4: Construct and utilize the basic functional blocks to design combinational circuits.**

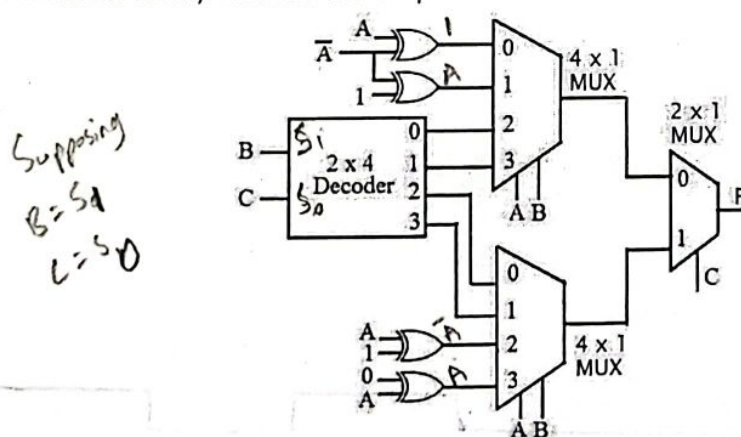**Q 1: (a)** For the logic diagram shown below, write down the output function F in  $\Sigma$  notation (Sum of Minterms form). Reduce the output function F in SOP. [10+5]



- (b) Use a 4 x 1 Multiplexer (with minimum added logic) to implement the following 4-variable Boolean Function:  $F(A, B, C, D) = \Sigma m(2, 3, 4, 6, 11, 12)$  [10]

# National University of Computer and Emerging Sciences Lahore Campus

## CLO# 4: Construct and utilize the basic functional blocks to design combinational circuits.

**Q 2:** Use a single decoder and a minimum number of OR gates to implement the following two Boolean Functions. Don't forget to mention the size of the decoder.

[10]

$$X(A, B, C) = (A + C') \cdot (B' + C)$$

$$Y(A, B, C) = A \cdot B' + B \cdot C$$


## CLO# 5: Design and demonstrate synchronous/ asynchronous digital circuits

**Q 3:** A new type of latch called KG latch has been introduced that is shown in the figure below:  
Solve this question here and attach this question paper with answer sheet.

(a) Fill-in the Next State Column of the function table of KG Latch.

[5]

Latch Inputs		Next State
K	G	Q(t+1)
0	0	Q(t)
0	1	Q(t)
1	0	0
1	1	1

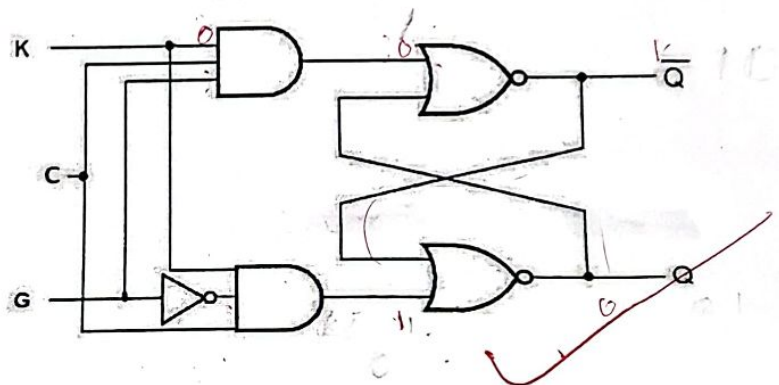

(b) Derive the characteristic equation  $Q(t+1)$  as a function of  $Q(t)$ ,  $K$ , and  $G$ .

[5]

$$Q(t+1) = KG + \bar{K}\bar{G}Q(t) + \bar{K}GQ(t)$$

$$Q(t+1) = KG + \bar{K}Q(t)$$

(c) Show the timing behavior of KG latch in the space below:

[5]

