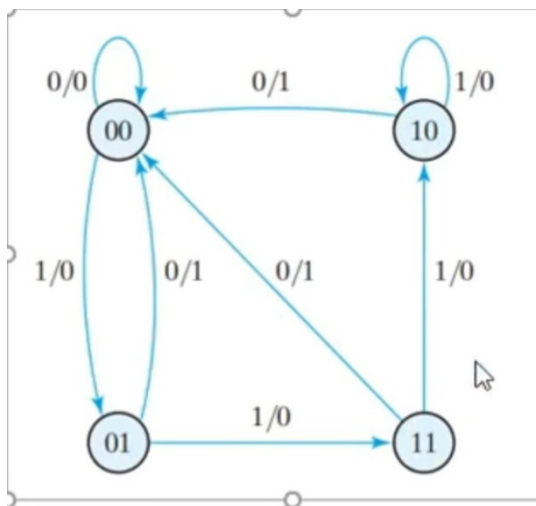




Course:	Digital Logic Design Lab	Course Code:	EL-227
Program:	BS(Computer Science)	Total Marks:	15
Duration:	35 minutes	Page(s):	1
Paper Date:	6 May 2023		
Section:	BDS 2A		
Exam:	Quiz-II		

QUESTION 1 : ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS WITH D FLIP FLOPS.State diagram is given below



- State table (2.5)
- INPUT EQUATIONS and Output equation (2.5)
- Implement it on logic works and show it to instructor. (10)