

# National University of Computer and Emerging Sciences, Lahore Campus



Course:  
Program:  
Duration:  
Date  
Section:

Digital Logic Design Lab  
BS (Computer Science)  
25 mins  
05-03-18  
B-2

Course Code: EL227  
Semester: Spring 2018  
Total Marks: 15  
Weight: 5%  
Pages: 2

## Question # 1

$$F = xy + x'y' + y'z \quad \text{Eq: (1)}$$

- a. Fill in the truth table of function given above.


Inputs			Output
X	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- b. Write Equation of Function in POS form (algebraic expression):


**M (A, B, C) =** \_\_\_\_\_  $(x' + y + z)$   
 $(x+y')$  \_\_\_\_\_

- c. Draw Circuit Diagram of Equation (1)

**Note: Use 2-input AND Gates**

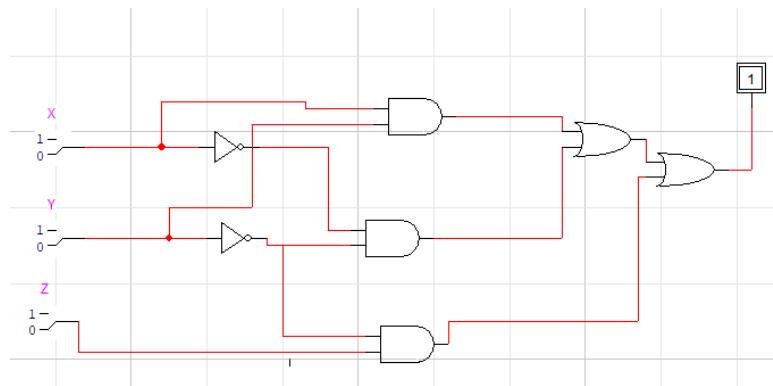

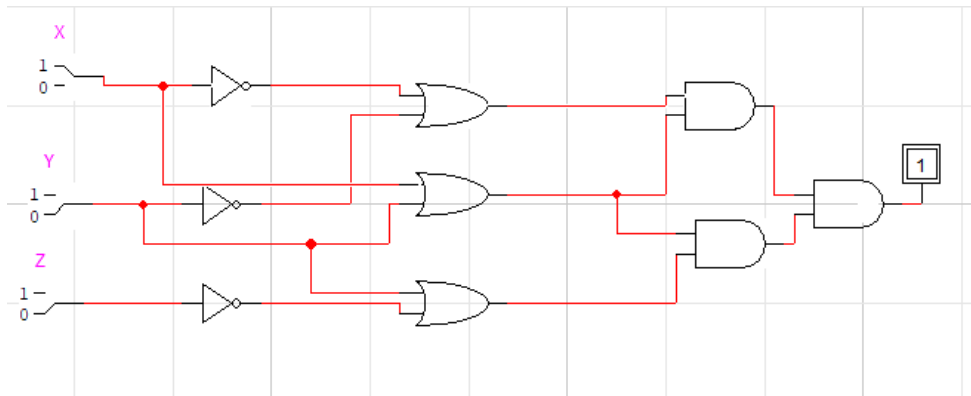- d. Draw Circuit Diagram of Equation (1) using **OR** and **NOT** Gates.  
**Note: Use 2-input OR Gates only**



- e. Apply Boolean Simplification Techniques to equation derived in Part (b) and show that the simplified equation is same as Equation (1).

$$(x' + y + z)(x + y')$$

$$\downarrow (xx' + x'y' + xy + yy' + xz + zy')$$

$$\downarrow (0 + x'y' + xy + 0 + y'z)$$

$$\downarrow xy + x'y' + y'z$$