
 


EE1005 – Digital Logic Design
Assignment#3 (CLO-05)

Due Date: May 14, 2024

 Question#1: Complete the timing diagram for the logic circuit given below: **Points: 20**

Note: Assume that the initial value of **F** is zero.



Characteristic tables for SR and D flip-flops:

C	S	R	Q(t+1)
0	X	X	Q(t) No change
1	0	0	Q(t) No change
1	0	1	0
1	1	0	1
1	1	1	Invalid

C	D	Q(t+1)
0	X	Q(t) No change
1	0	0
1	1	1

Question#2:

Points : 20

For the synchronous sequential circuit shown in figure 1, do the following:

- Determine expressions for the flip-flop inputs **J1**, **K1** and the output function **Z**.
- Find state table.
- Draw the state diagram.
- State that whether the model is Mealy or Moore.


 
 


Figure 1

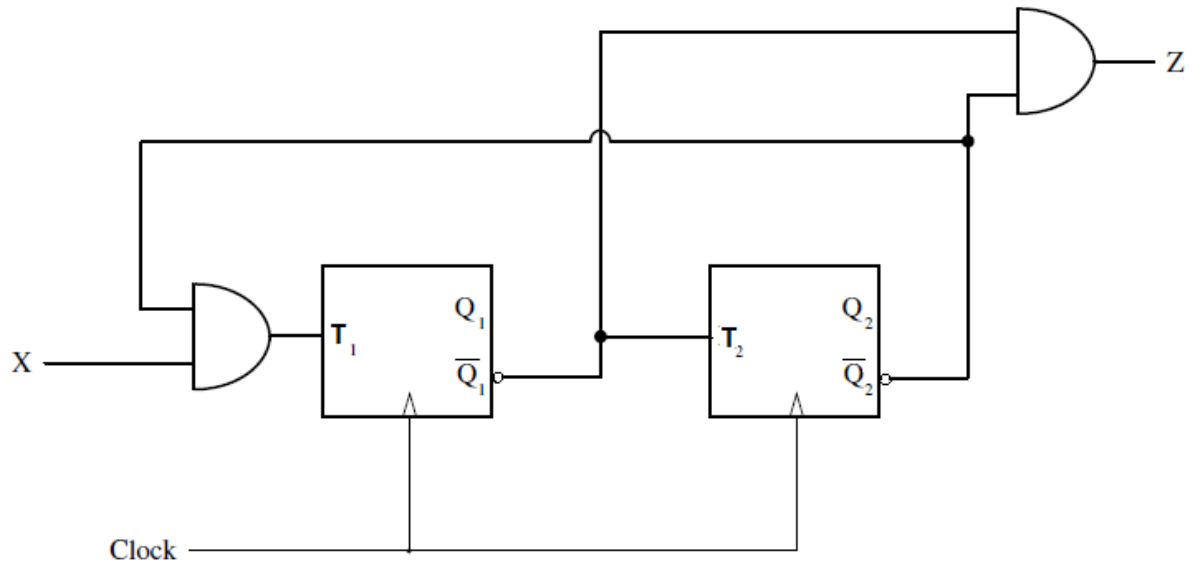Question#3:

Points : 20

Complete the timing diagram given below for the following synchronous sequential logic circuit.



Question#4:

Points: 30

Design a synchronous binary arbitrary counter to produce the sequence 1, 4, 3, 5, 7, 6, 2, 1 and so on.

- Find the state diagram and state table for the required circuit.
- State that whether the model is Mealy or Moore.
- Find an implementation of the circuit using positive edge triggered D flip flops and logic gates.
- A counter is self-correcting if, after entering an unused state, it eventually returns to its proper count sequence. Is your designed counter shows self-correction behavior?

Question#5:

Points: 30

A serial leading-1s detector is to be designed. A binary integer of arbitrary length is presented to the serial leading-1s detector, most significant bit first, on input X . As long as the bits applied to X are 0, $Z = 0$. When the first 1 is applied to X , $Z = 1$. For all bit values applied to X after the first 1 is applied, $Z = 0$. To indicate that the sequence is complete and that the circuit is to be initialized to receive another sequence, input Y becomes 1. Otherwise, Y is 0.

- Find the state diagram and state table for the required circuit.
- State that whether the model is Mealy or Moore.
- Find an implementation of the circuit using positive edge triggered D flip flops and logic gates.

Question#6:

Points: 30

A Universal Serial Bus (USB) communication link requires a circuit that produces the sequence **00000001**. You are required to design a circuit that starts producing this sequence if the input $E = 1$. If $E = 0$, the output remains constant at 1.

Once the sequence starts, it does not see input E until the sequence is complete. When the sequence completes, it will see the input E .

- Find the state diagram and state table for the required circuit.
- State that whether the model is Mealy or Moore.
- Find an implementation of the circuit using positive edge triggered D flip flops and logic gates.