

# Digital Logic Design (EE1005)

Date: February 28, 2024

Course Instructor(s)

Ms. Sobia Tariq Javed

Ms. Maimona Akram

Dr. Amjad Hussian

Mr. Amjad Ali

Mr. Aftab Alam

Mr. Zummar Saad

## Sessional-I Exam

Total Time: 1 Hours

Total Marks: 50

Total Questions: 04

Semester: SP-2024

Campus: Lahore

Dept: Computer Science

Q1 Q2 Q3 Q4  
10 10 20 10

Student Name

Roll No

Section

Student Signature

Vetted by

Vetter Signature

CLO#1: Understand different number systems and their conversion.

Q#1:  $(236.25)_7 + (102)_3 = (253.25)_7$ 

[10 marks]

$$\begin{array}{r} 236.25 \\ + 14 \\ \hline 253.25 \end{array}$$

$$6+4 = 10 - 7 = 3$$

$$\begin{array}{r} 2 \times 3^0 = 2 \\ + 0 \times 3^1 = 0 \\ + 1 \times 3^2 = 9 \\ \hline (11)_3 \end{array}$$


$$\begin{array}{r} 7 \overline{) 11} \\ 7 \phantom{0} \\ \hline 4 \end{array}$$

$$(14)_7$$

CLO#2: Recognize and use basic gates to implement logic circuits


Q#2: Redraw the following logic diagram with the reduced number of gates. Available resources are 2-input (AND, OR, XOR) and NOT gate.
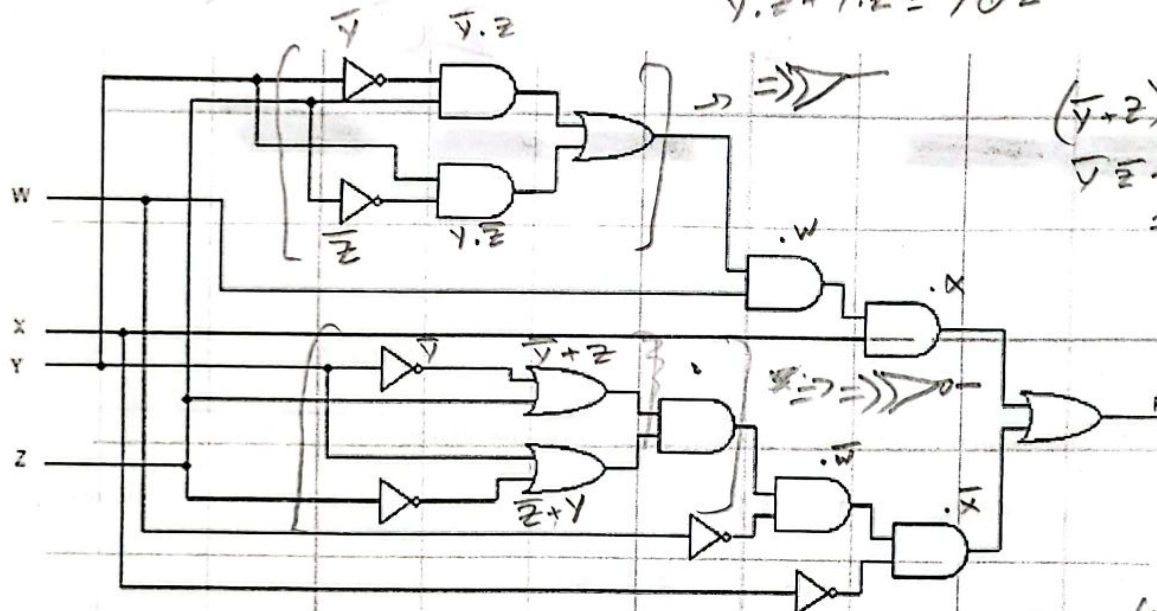
$$\bar{Y} \cdot Z + Y \cdot \bar{Z} = Y \oplus Z \quad [10 \text{ marks}]$$



$$\begin{aligned} &(\bar{Y} + Z)(\bar{Z} + Y) \\ &\bar{Y}\bar{Z} + \bar{Y}Y + Z\bar{Z} + ZY \\ &= \bar{Y}\bar{Z} + 0 + 0 + ZY \\ &= \bar{Y}\bar{Z} + ZY \end{aligned}$$
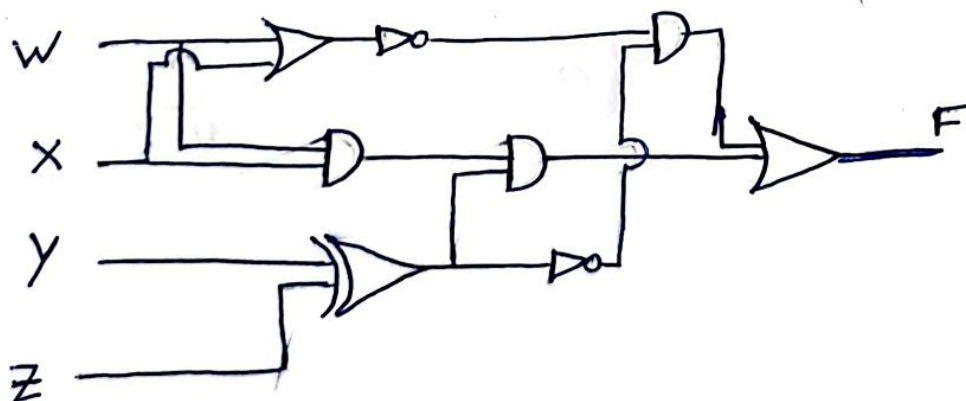
$$(Y \oplus Z)(WX) + (\overline{Y \oplus Z})(\overline{WX})$$



CLO#3: Constructs optimized logic circuit design.

Q#3: A Boolean function is given as follows:

[10+10 marks]

$$F(A, C, B, D) = \prod M(1, 4, 9, 11, 12)$$

Don't care:  $d(A, C, B, D) = \sum m(2, 3, 5, 7, 8)$

(Note: No marks will be given if K-map is not properly filled.)

- Minimize the function  $F$  in Product of Sums form using K-maps shown below:

$$F(A, C, B, D) = (\bar{C} + B + D)(C + \bar{D})$$

(10)

AC \ BD	00	01	11	10
00	0	0	X	X
01	0	X	X	
11	0			
10	X	0	0	


$$(\bar{C} + B + D)$$

$$(C + \bar{D})$$



- Minimize the function  $F$  in Sum of Products form using K-maps shown below:
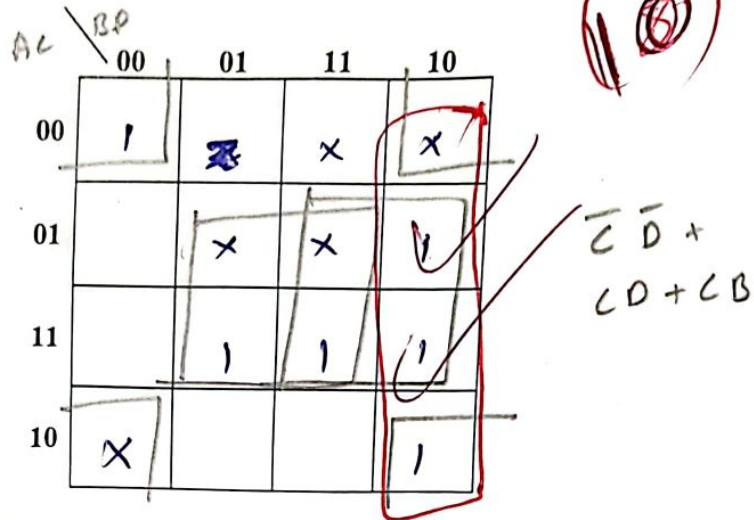
$$F(A, C, B, D) = \underline{\bar{C}\bar{D} + CD + CB}$$



**CLO#4:** Construct and utilize the basic functional blocks to design combinational circuits

**Q#4:** A combinational circuit is required to be designed for coordinating a meeting among four parties (A, B, C, and D). The circuit should output 'F=1' if meeting can take place while ensuring that either party A or D must be present, and the meeting can only be scheduled if at least two parties express their willingness to attend. Otherwise, the meeting cannot take place i.e., 'F=0'. You don't need to draw the circuit. Only fill-in the truth table and write down the Boolean expression of function  $F$  in Sum of Minterms form (SOP). Do not optimize the expression. [10 marks]

(Note: The presence and willingness of a party is represented by high logic level)

Inputs				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$F(A, B, C, D) = \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BCD + \bar{A}B\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$$

Simplified (Extra):-

$$AB + CD + BD + AD + AC$$