

Course:	Digital Logic Design	Course Code:	EE1005
Program:	BS(Computer Science/ Data Science)	Semester:	Spring 2022
Duration:	60 Minutes	Total Marks:	50
Paper Date:	24/03/2022	Weight	15%
Section:	ALL	Page(s):	4
Exam:	Midterm-I	Roll No.	
		Section:	

- Instruction/Notes:
- Attempt all the questions on this answer booklet.
 - Make sure to write down your roll # on EVERY sheet in the given space.
 - Use of calculator is not allowed.

Question 1 [10 Marks]: Determine the value of the radix r if $(112)_r = (1012)_3$

$(1012)_3$ Convert it in decimal

$$1 \times 3^3 + 0 \times 3^2 + 1 \times 3^1 + 2 \times 3^0$$

$$27 + 3 + 2 = (32)_{10}$$

Now $(112)_r$ convert it in Base 5

$$1 \times 5^2 + 1 \times 5^1 + 2 \times 5^0$$

$$25 + 5 + 2 = (32)_5$$

It means if $(112)_r = (1012)_3$

So $r = 5$

10

Question 2 [10 + 6 = 16 Marks]: Design a combinational circuit with a 4-bit input. The 4-bit input represents the month number, 0001 for January, 0010 for February, 0011 for March and so on. The circuit has three outputs F_2 , F_1 , F_0 as shown in Figure 1.

J 0001
F 0010
M 0011
A 0000

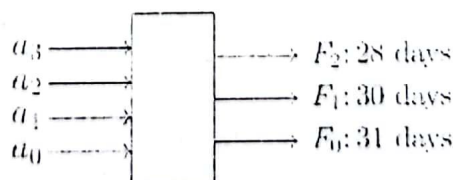


Figure 1: Number of days calculator.

The output F_2 is 1 if the input month has 28 days.

The output F_1 is 1 if the input month has 30 days,

and output F_0 is 1 if the input month has 31 days. Ignore the leap year.

For invalid inputs, it doesn't matter what's the output.

(a) Fill-in the entries for the outputs in the truth table shown below:

Inputs				Outputs		
a_3	a_2	a_1	a_0	F_2	F_1	F_0
0	0	0	0	x	x	x
30 J	0	0	1	0	1 0	0 1
28 F	0	1	0	1	0	0
31 M	0	1	1	0	0	1
30 A	0	1	0	0	1	0
31 Mar	0	1	1	0	0	1
30 J	0	1	0	0	1	0
31 Ji	0	1	1	0	0	1
31 Aug	1	0	0	0	0	1
30 Sep	1	0	1	0	1	0
31 Oct	1	0	0	0	0	1
30 Nov	1	0	1	0	1	0
31 Dec	1	1	0	0	0	1
	1	1	1	x	x	x
	1	1	0	x	x	x
	1	1	1	x	x	x

(b) Write the function F_2 and F_0 in Sum of Minterms form and F_1 in Product of Maxterm form.

$$F_2(a_3, a_2, a_1, a_0) = \sum m(2)$$

$$F_1(a_3, a_2, a_1, a_0) = \prod M(2, 3, 5, 7, 8, 10, 12)$$

$$F_0(a_3, a_2, a_1, a_0) = \sum m(1, 3, 5, 7, 8, 10, 12)$$

12+3

9

Roll # 212-5401

Question 3 [4 + 10 + 10 = 24 Marks]: A Boolean function is given as follows:

$$F(A, B, C, D) = AC' + B'D + A'CD + ABCD$$

a) Write down the function F in Sum of Minterms and Product of Maxterm form.

$$F(A, B, C, D) = \sum m(1, 3, 7, 8, 9, 11, 12, 14, 15, 13)$$

$$F(A, B, C, D) = \prod M(0, 4, 2, 5, 6, 10, 14)$$

b) Minimize the function F in Sum of Products form using K-maps shown below:

AB \ CD	00	10	11	01
00	0	1	1	0
10	0	0	1	0
11	1	1	1	1
01	1	1	1	0

Wrongly placed.
5

$$F(A, B, C, D) = \cancel{ABC' + CD + A'BD'} + AB + CD + A'B'C + A'BD'$$

c) Minimize the function F in Product of Sums form using K-maps shown below:

AB \ CD	00	10	11	01
00	0	0		0
10	0	0		0
11		0		
01				0

AB \ CD	00	01	11	10
00	0			0
01	0	0		0
11				
10				0

$$F(A, B, C, D) = \cancel{(B + D) \cdot (A' + CD) \cdot (A + CD') \cdot (B + CD')} \\ \cancel{(A + CD) \cdot (A + C) \cdot (A + D)}$$

NOT P.O.S form.