


# National University of Computer and Emerging Sciences, Lahore Campus

	Course Name:	Computer Architecture	Course Code:	EE204
	Program:	BS(Computer Science)	Semester:	Fall 2018
	Duration:	60 Minutes	Total Marks:	30
	Paper Date:	01-10-2018	Weight	15
	Exam Type:	Midterm I	Page(s):	4

**Student : Name:** \_\_\_\_\_ **Roll No.** \_\_\_\_\_

**Section:** \_\_\_\_\_

**NOTE:** Answer in the space provided. You can ask for rough sheets but they won't be graded.

## Question 1 [8] Encircle the right answer.


- There are 32 general purpose registers. So a machine instruction must use a bit field of what size to designate a register?
  - 3
  - 4
  - 5
  - 16
- How many bits are there in each MIPS machine instruction?
  - 8
  - 16
  - 32
  - Different instructions are of different lengths
- Consider the following 32-bit j instruction 000010 00 0001 0000 0000 0000 0000 1000. The first 6 bits are the op-code and rests of the 26 bits are allocated for jump address. Here is the value of the PC+4 while the target address is being constructed: 0000 1000 0001 0000 0000 1100 0110 1000.  
What address does the j put into the PC?
  - 0000 1000 0001 0000 0000 1100 0110 1000
  - 0000 10 0001 0000 0000 1100 0110 1000 00
  - 0000 00 0001 0000 0000 0000 0000 1000 00
  - 1000 00 0001 0000 0000 0000 0000 1000 00
- The value of the function field (funct) for lw and sw instructions is:
  - 0
  - 10
  - 34
  - Not applicable
- A 3-to-8 decoder can be constructed with \_\_\_\_\_ 2-to-4 decoders:
  - 1
  - 2
  - 3
  - 4
- A combinational circuit that receives binary information from one of  $2^n$  input data lines and directs it to a single output line is called:
  - Decoder
  - Multiplexer
  - Flip-flop
  - Binary Counter
- An overflow can be detected while performing arithmetic left shift by the following condition. Here  $R_{n-1}$  represents the MSB while  $R_0$  represents the LSB.
  - $R_{n-1} \wedge R_{n-2}$  (AND)
  - $R_{n-1} \oplus R_{n-2}$
  - $R_{n-1} \vee R_{n-2}$  (OR)
  - $R_0 \oplus R_1$

8. In binary adder-subtractor, the addition and subtraction can be combined into one common circuit by including a/an \_\_\_\_\_ gate with each full adder:
- OR gate
  - XOR gate
  - NOR gate
  - NOT gate (inverter)
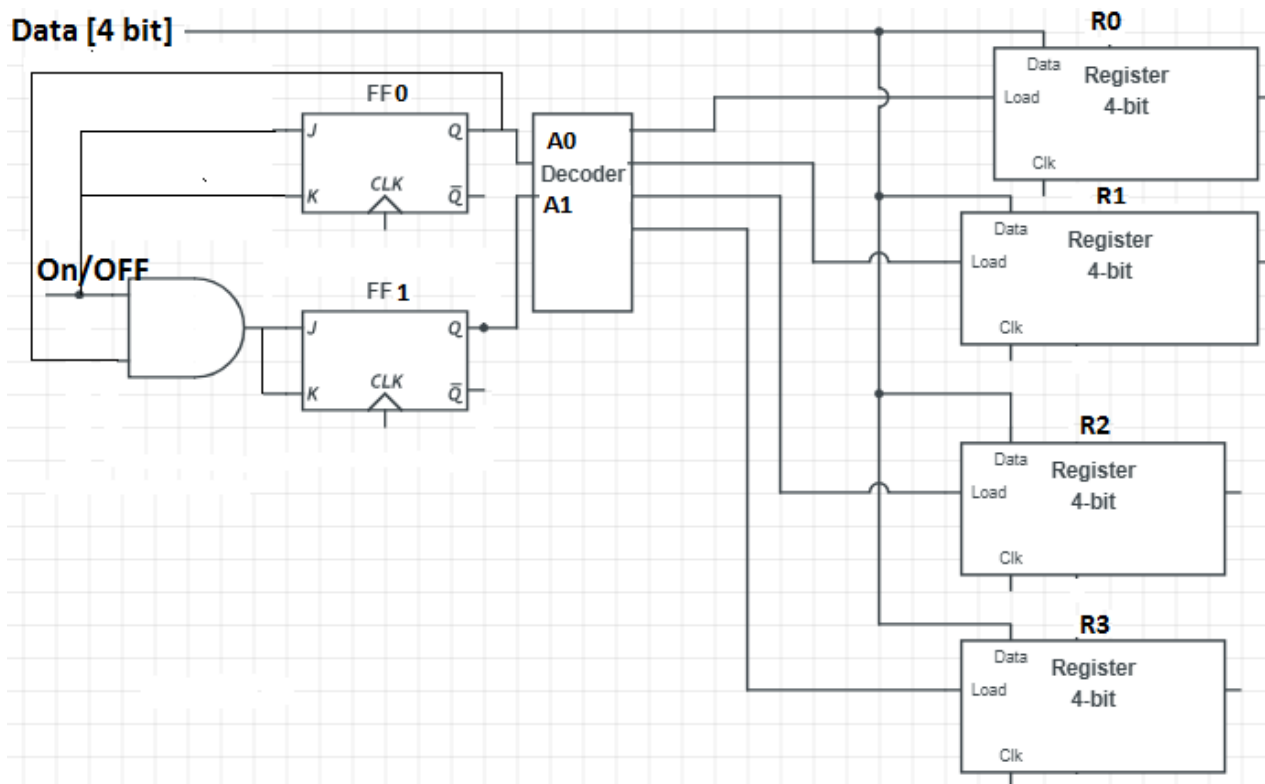
## Question 2 [8]

Consider the circuit below.

- FF0 and FF1 are JK Flip Flops and both are initialized to 0.
- All the circuit components are attached to the same clock (Although it is not mentioned in the circuit below)
- Each register(R0-R3) is 4 bit and the decoder is 2 x 4



Initial values for the registers are as follows

R0	1011
R1	0101
R2	1001
R3	0010

Following is the input to the circuit for next 5 Clock Cycles

- Clock Cycle 1: ON/OFF : 1, Data: 0000
- Clock Cycle 2: ON/OFF : 1, Data: 0000
- Clock Cycle 3: ON/OFF : 1, Data: 1100
- Clock Cycle 4: ON/OFF : 1, Data: 1100
- Clock Cycle 5: ON/OFF : 1, Data: 1111

What are the contents of the registers after Clock Cycle 5? Fill in the table below to answer the question.

R0	<b>1100</b>
R1	<b>1111</b>
R2	<b>0000</b>

Suppose we want to add support for the following instruction in our MIPS architecture.

- c. For this instruction, specify the value of all control signals shown in the diagram plus any additional signals you may have added. Name the signal and briefly describe its purpose in the table below.

Control Signal	Value	Description
ALUOp	00	2 bit value to ALU control for BeqM instruction
RegDst	x	
Branch	0	
MemRead	1	
MemWrite	0	
MemToReg	x	
AluSrc	0	
RegWrite	0	
BeqM	1	If this signal is 1 and $Rt == Mem[Offs + Rs]$ then set $PC == Rt$

- d. If each register contain the value equal to its register number (R4 contains value 4 etc.) and in Data memory at each address, value is double of its address (at address2, value is 4 and at address3, value is 6 etc.) then what would be the value of *rt* after the completion of **BeqM** instruction.

**The value of *rt* is simply the value stored in register *rt* ( $R9 == 9$ )**