

EE1005 – Digital Logic Design (BCS-2E, BCS-2F, BDS-2A)

Assignment#2

CLO-04


Due Date: April 4, 2024

Total Marks: 160

 Question#1:

[Marks: 10]

Find the truth table for the outputs Y0, Y1, and Y2.



Question#2:

[Marks: 20]

Design a combinational circuit, using **2x1 multiplexers**, that accepts a 3-bit number as input and generates a 2-bit binary number as output that approximates the square root of the input number. For example, if square root is ≥ 2.5 , give a result of 3. If the square root is < 2.5 and ≥ 1.5 , give a result of 2.

Note: Use minimum additional logic along with 2x1 MUXs.

Question#3:

[Marks: 20]

Design a combinational circuit that takes 3-bit pattern as input and outputs binary code of bit position of the first '1' in the pattern reading from MSB (2^{nd} position) to LSB (0^{th} position). An additional output variable **V** is required along with binary code to indicate that the binary code is valid or not i.e., if the input pattern is '000' then the output **V** should be '0' to indicate that the

binary code is not indicating the bit position of first '1' and we don't care about the binary code if $V = 0$.

Design the required circuit using dual 4x1 MUXs and minimum additional logic. Available resources along with **dual 4x1 MUXs** are **NOT gates, 2-input (AND, OR, NAND, NOR) gates**.

Question#4:

[Marks: 20]

- a) Design a 32x1 MUX with active low enable using dual 4x1 MUXs with active low enables and 2x1 MUX with low enable. Use minimum extra logic to design the required MUX.
- b) Implement following Boolean functions using 16x1 MUX
 - i. $F_1(A, B, C, D) = \sum m(1, 2, 5, 6, 11, 12, 15)$
 - ii. $F_2(A, B, C, D, E) = \sum m(1, 2, 5, 6, 16, 19, 20, 21, 22, 23, 27, 30, 31)$

Question#5:

[Marks: 30]

- a) Design a 5x32 decoder using 3x8 and 2x4 decoders with active low enables and active high outputs. Use minimum extra logic to design the required decoder.
- b) Add active low enable to 5x32 decoder designed in part (a).
- c) Implement following Boolean functions using 5x32 decoder. Use minimum extra logic. Available resources are NOT, AND, OR, NAND, NOR gates. Available input pins for each gate are 3, 6, 8 (except NOT gate).
 - i. $F_1(A, B, C, D, E) = \sum m(0, \dots, 25)$
 - ii. $F_2(A, B, C, D, E) = \sum m(6, 7, 8, 9, 16, 24, 27, 29)$
 - iii. $F_2(A, B, C, D, E) = \sum m(1, 2, 6, 7, 8, 20, 24, 26, 28, 30)$


Question#6:

[20 marks]

Design an optimized combinational circuit to perform the arithmetic operation $(3x + 6y + 9)$. Here, x (2-bit) and y (3-bit) are two unsigned numbers. Available resources are **4-bit Adders, Full Adders (FA), NOT gates, 2-input (AND, OR, NAND, NOR) gates**. Show complete working.

 Question#7:

The Selector Box below has two 4-bit, unsigned inputs, A and B . Its output is $Z = A+2$ if $A \geq B$ and $Z = B+2$ if $A < B$. [20 marks]



Question#8:

Design a logic circuit that performs the following operations on A (3-bit number) and B (3-bit number) according to the status of selection bits S_1 and S_0 : [20 marks]

S_1S_0	Operation	F (Output)
00	Incrementer	$A+1$
01	Tripler	$3*A$
10	Multiplier	$A*B$
11	Square	A^2