

National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design
 Program: BS (Computer Science)
 Duration: 20 Minutes
 Paper Date: 14-June-21
 Section: 2F
 Exam: Quiz 1

Course Code: EE-227
 Semester: Spring 2021
 Total Marks: 20
 Weight: 3 %
 Page(s): 3
 Reg. No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

Solution

[10M]

Question 01:

Characteristic table of NP Flip-Flop is given below:

- Write the Characteristic equation of NP Flip-Flop. Show your working to get credit.
- Fill in the excitation table of NP Flip Flop.
- Draw its circuit.

Characteristic Table of NP Flip-Flop

N	P	$Q(t+1)$
0	0	0
0	1	$Q(t)$
1	0	$Q(t)'$
1	1	1

Excitation Table of NP Flip-Flop

$Q(t)$	$Q(t+1)$	N	P
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

Characteristic Equation of NP Flip-Flop:

$$Q(t+1) = \overline{Q}N + QP$$

Circuit Diagram of NP Flipflop

Draw yourself

Question 02:


A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:

$$DA = XA + X'Y'$$

$$DB = XB + X'A,$$

$$Z = X'B$$

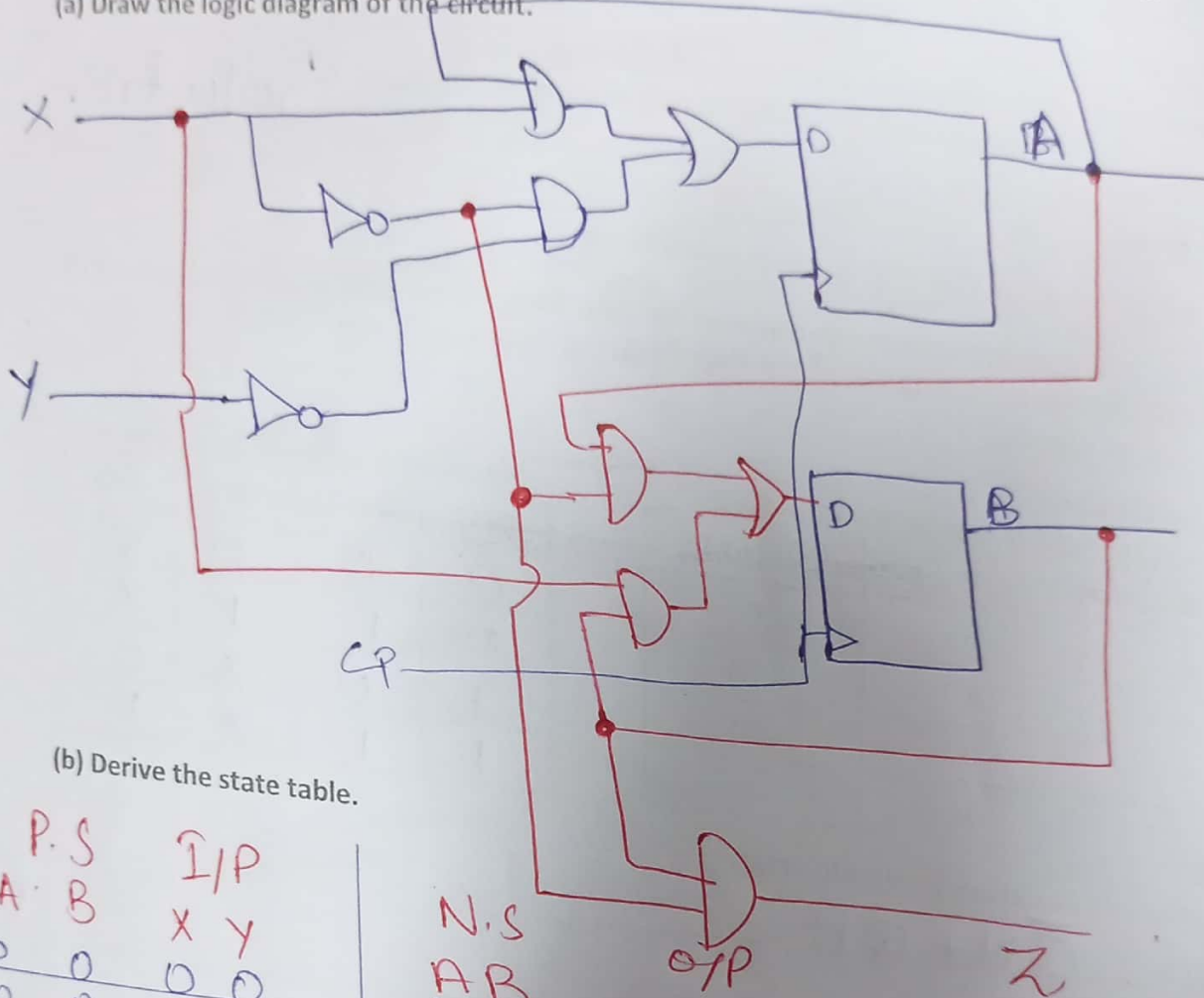
(a) Draw the logic diagram of the circuit.



(b) Derive the state table.

P.S		I/P		N.S		O/P
A	B	X	Y	A	B	
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	1	0	1
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	1	0
1	0	0	1	1	1	0
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	1	1	1
1	1	0	1	0	1	1
1	1	1	0	1	1	0
1	1	1	1	1	1	0

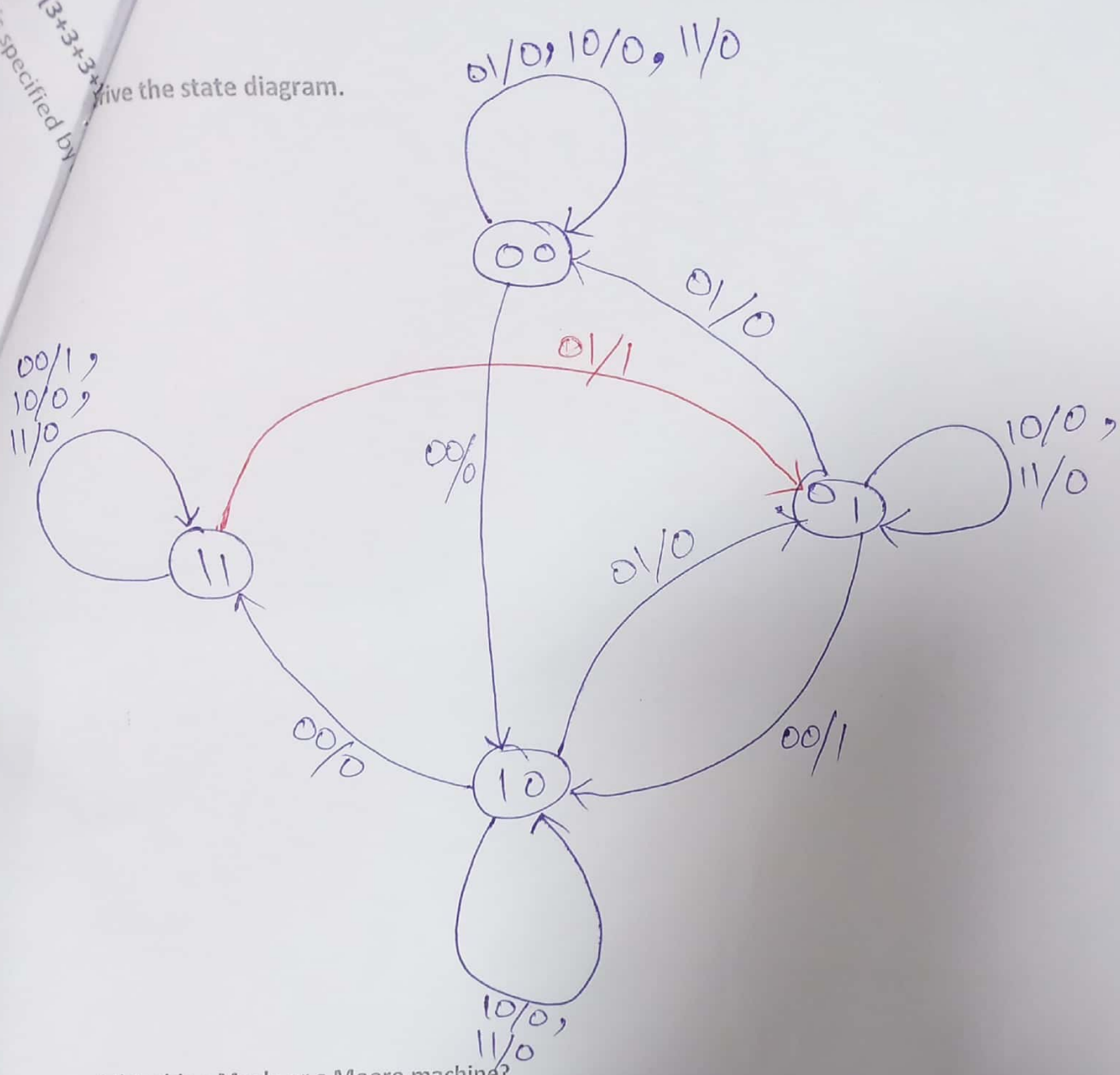is specified by [3+3+3+3] Give the state diagram.



(d) Is this a Mealy or a Moore machine?

Mealy - (output is dependant on Present state as well as input)

National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design
Program: BS (Computer Science)
Duration: 20 Minutes
Paper Date: 14-June-21
Section: 2E
Exam: Quiz 1

Course Code: EE-227
Semester: Spring 2021
Total Marks: 20
Weight: 3 %
Page(s): 3
Reg. No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

Solution

[10M]

Question 01:

Characteristic table of L-M Flip Flop is given below. Find its characteristic equation and draw the circuit diagram.

- Write the Characteristic equation of LM Flip-Flop. Show your working to get credit.
- Fill in the excitation table of LM Flip Flop.
- Draw its circuit.

Characteristic Table of NP Flip-Flop

L	M	$Q(t+1)$
0	0	$Q'(t)$
0	1	1
1	0	$Q(t)$
1	1	0

Excitation Table of LM Flip-Flop

$Q(t)$	$Q(t+1)$	L	M
0	0	1	X
0	1	0	X
1	0	X	X
1	1	X	X

Characteristic Equation of LM Flip-Flop:

$$Q(t+1) = \underline{\bar{Q}\bar{L} + \bar{L}M + QL\bar{M}}$$

Circuit Diagram of LM Flipflop

Draw yourself

Question 02:


A sequential circuit with two D flip-flops A and B, one input Y, and one output Z is specified by the following input equations:

$$DA = BY + A'Y,$$

$$DB = Y',$$

$$Z = A'B'$$

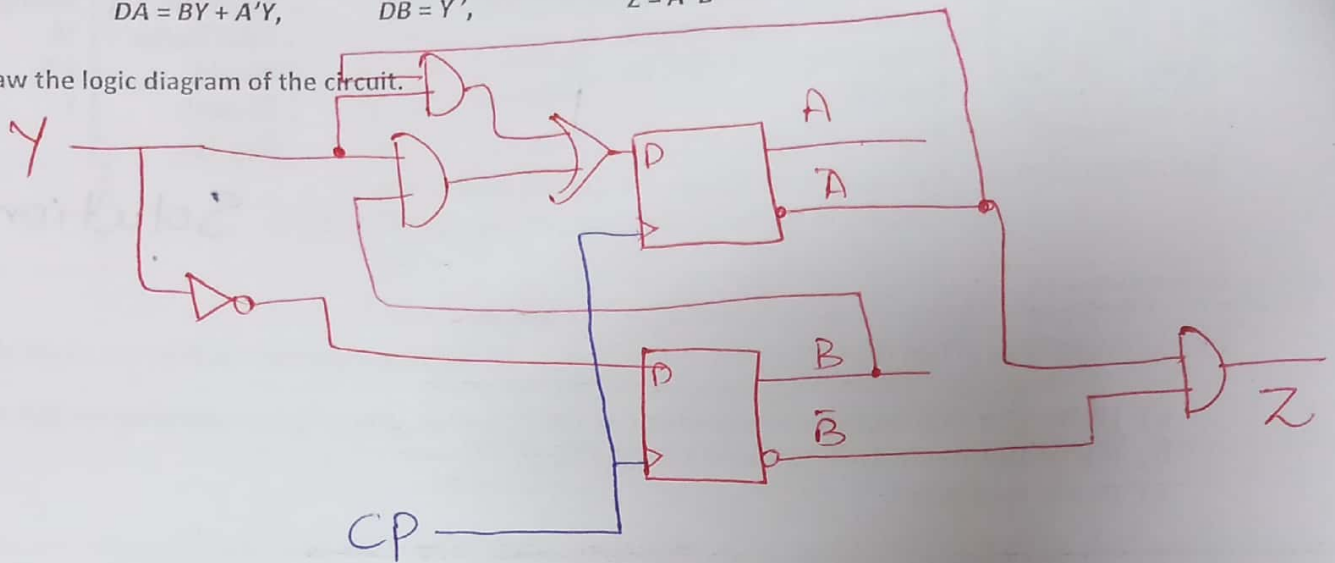
(a) Draw the logic diagram of the circuit.



(b) Derive the state table.

P.	S	I/P	N.S	Output	
A	B	Y	A	B	Z
0	0	0	0	1	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	1	0
1	1	1	1	0	0

(c) Derive the state diagram.

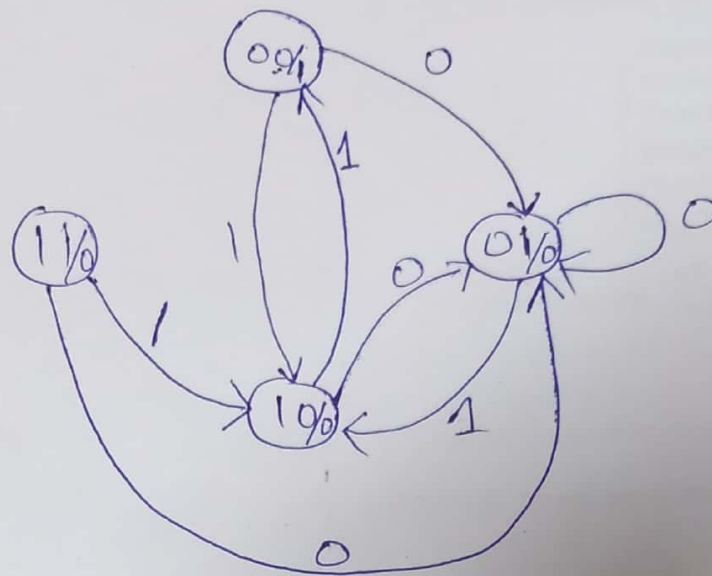

(d) Is this a Mealy or a Moore machine?

Moore machine

(output is dependent on present state)

National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design
 Program: BS (Computer Science)
 Duration: 15 Minutes
 Paper Date: 16-June-21
 Section: 2F
 Exam: Quiz 2

Course Code: EE-227
 Semester: Spring-2021
 Total Marks: 15
 Weight: 2.5 %
 Page(s): 2
 Roll No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

[5 M]

Question 01:

Simplify following combinational circuits using Boolean algebra identities and rules.

Note: Show all steps of simplification and mention which the laws used for simplification in each step.

$$AB'C + A'BC + A'B'C$$

$$= A\bar{B}C + \bar{A}C(B + \bar{B})$$

$$\because a + \bar{a} = 1$$

$$= A\bar{B}C + \bar{A}C$$

$$= C(A\bar{B} + \bar{A})$$

$$\because a + \bar{a}b = a + b$$

$$= C(A + \bar{A})(\bar{B} + \bar{A})$$

$$\because A + \bar{A} = 1$$

$$= C(\bar{B} + \bar{A})$$

Question 02:

Optimize the following functions into (1) sum-of-products and (2) product-of-sums forms:

$$F(A, B, C, D) = (A' + B' + D')(A + B' + C')(A' + B + D')(B + C' + D')$$

(a) Write the above function in

$$\text{Sum of Product (SOP)} = \sum m(0, 1, 2, 4, 5, 8, 10, 12, 14)$$

$$\text{Product of Sum (POS)} = \prod M(3, 6, 7, 9, 11, 13, 15)$$

(b) Use only given K-Maps to simplify (optimize) the function into:

(i) Sum of Product (SOP) form

AB \ CD	00	01	11	10
00	1	1	0	1
01	1	1	0	0
11	1	0	0	1
10	1	0	0	1

$$F(A, B, C, D) = \bar{B}\bar{D} + \bar{C}\bar{D} + \bar{A}\bar{C}$$

(ii) Product of Sum (POS) form

AB \ CD	00	01	11	10
00	1	1	0	1
01	1	1	0	0
11	1	0	0	1
10	1	0	0	1

$$F(A, B, C, D) = (\bar{A} + \bar{D})(\bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C})$$

National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design
 Program: BS (Computer Science)
 Duration: 15 Minutes
 Paper Date: 16-June-21
 Section: 2E
 Exam: Quiz 2

Course Code: EE-227
 Semester: Spring 2021
 Total Marks: 15
 Weight: 2.5 %
 Page(s): 2
 Roll No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

Question 01:

[5 M]

Simplify following combinational circuits using Boolean algebra identities and rules.

Note: Show all steps of simplification and mention which the laws used for simplification in each step.

$$AB'C(BD + CDE) + AC'$$

$$= A\bar{B}BCD + A\bar{B}CDE + A\bar{C}$$

$$= 0 + A(\bar{B}CDE + \bar{C})$$

$$= A(C + \bar{C})(\bar{B}DE + \bar{C})$$

$$= A(\bar{C} + \bar{B}DE)$$

$$\therefore B \cdot \bar{B} = 0$$

$$\therefore x + \bar{x}y = x + y$$

$$\therefore C + \bar{C} = 1$$

[10 M]

Question 02:

Optimize the following functions into (1) sum-of-products and (2) product-of-sums forms:
 $F(A, B, C, D) = \sum m(2, 3, 5, 7, 8, 10, 12, 13)$

(a) Write the above function in

Sum of Product (SOP) =

$$(\bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D})$$

$$\text{Product of Sum (POS)} = ((A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D) \cdot (A+B+\bar{C}+D))$$

(b) Use only given K-Maps to simplify (optimize) the function into:

(i) Sum of Product (SOP) form

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	1	1	0	0
10	1	0	0	1

$$F(A, B, C, D) = \bar{A}\bar{C}\bar{D} + B\bar{C}\bar{D} + \bar{A}CD + \bar{B}C\bar{D}$$

(ii) Product of Sum (POS) form

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	1	1	0	0
10	1	0	0	1

$$F(A, B, C, D) = (A+B+C)(A+B+D)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{D})$$



Course: Digital Logic Design
 Program: BS (Computer Science)
 Duration: 15 Minutes
 Paper Date: 21-June-21
 Section: 2F
 Exam: Quiz 3


Course Code: EE-227
 Semester: Spring 2021
 Total Marks: 10
 Weight: 2.5 %
 Page(s): 2
 Roll No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

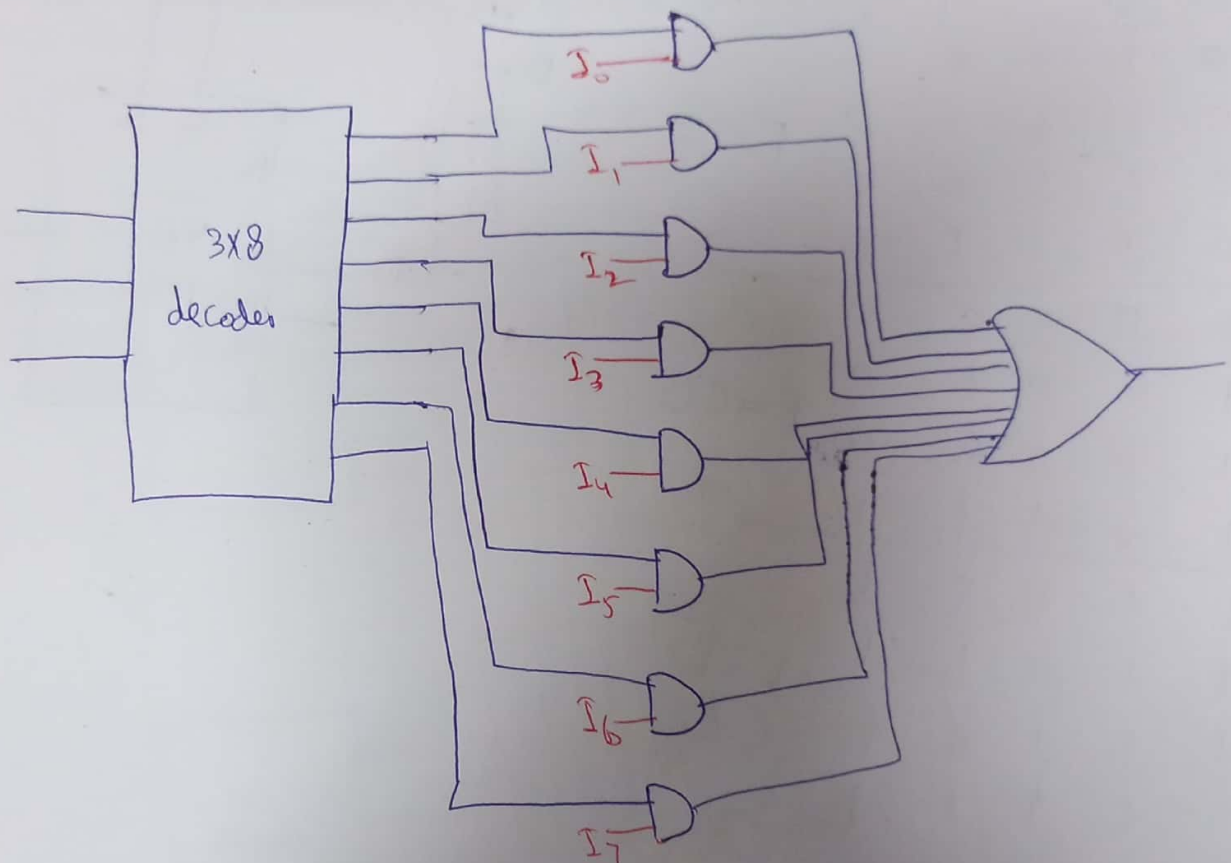Question 01:

[5 M]

Design an 8-to-1-line multiplexer using a 3-to-8-line decoder and an 8X2 AND-OR.



[5M]

Question 02:

Implement the Boolean function $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$ with a 4-to-1-line multiplexer and external gates. Connect inputs A and B to the selection lines. The input requirements for the four data lines will be a function of the variables C and D. The values of these variables are obtained by expressing F as a function of C and D for each of the four cases when AB = 00, 01, 10 and 11. These functions must be implemented with external gates.


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
<hr/>				
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
<hr/>				
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
<hr/>				
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$F = D$

$F = \bar{C}\bar{D}$

$F = CD$

$F = 1$

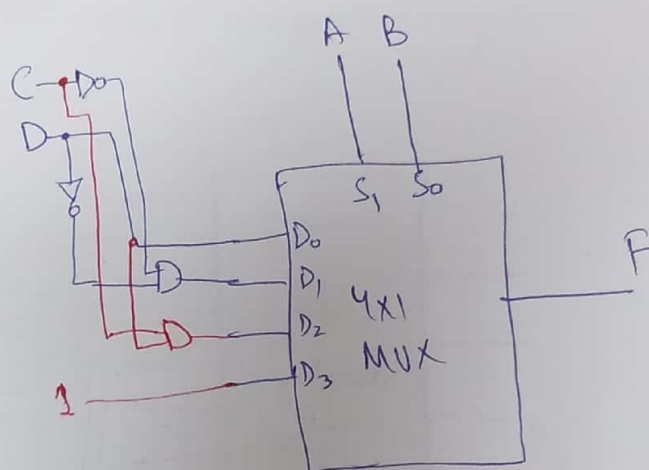



Course: Digital Logic Design
 Program: BS (Computer Science)
 Duration: 15 Minutes
 Paper Date: 21-June-21
 Section: 2E
 Exam: Quiz 3


Course Code: EE-227
 Semester: Spring 2021
 Total Marks: 15
 Weight: 2.5 %
 Page(s): 2
 Roll No.

Instruction/Notes: Calculators are strictly not allowed in all exams
 Plagiarism will be dealt seriously causing an F in course

Question 01:

[5 M]

Construct a 12-to-1-line multiplexer with a 3-to-8-line decoder, a 1-to-2-line decoder, and a 12x3 AND-OR. The selection codes 0000 through 1011 must be directly applied to the decoder inputs without added logic.

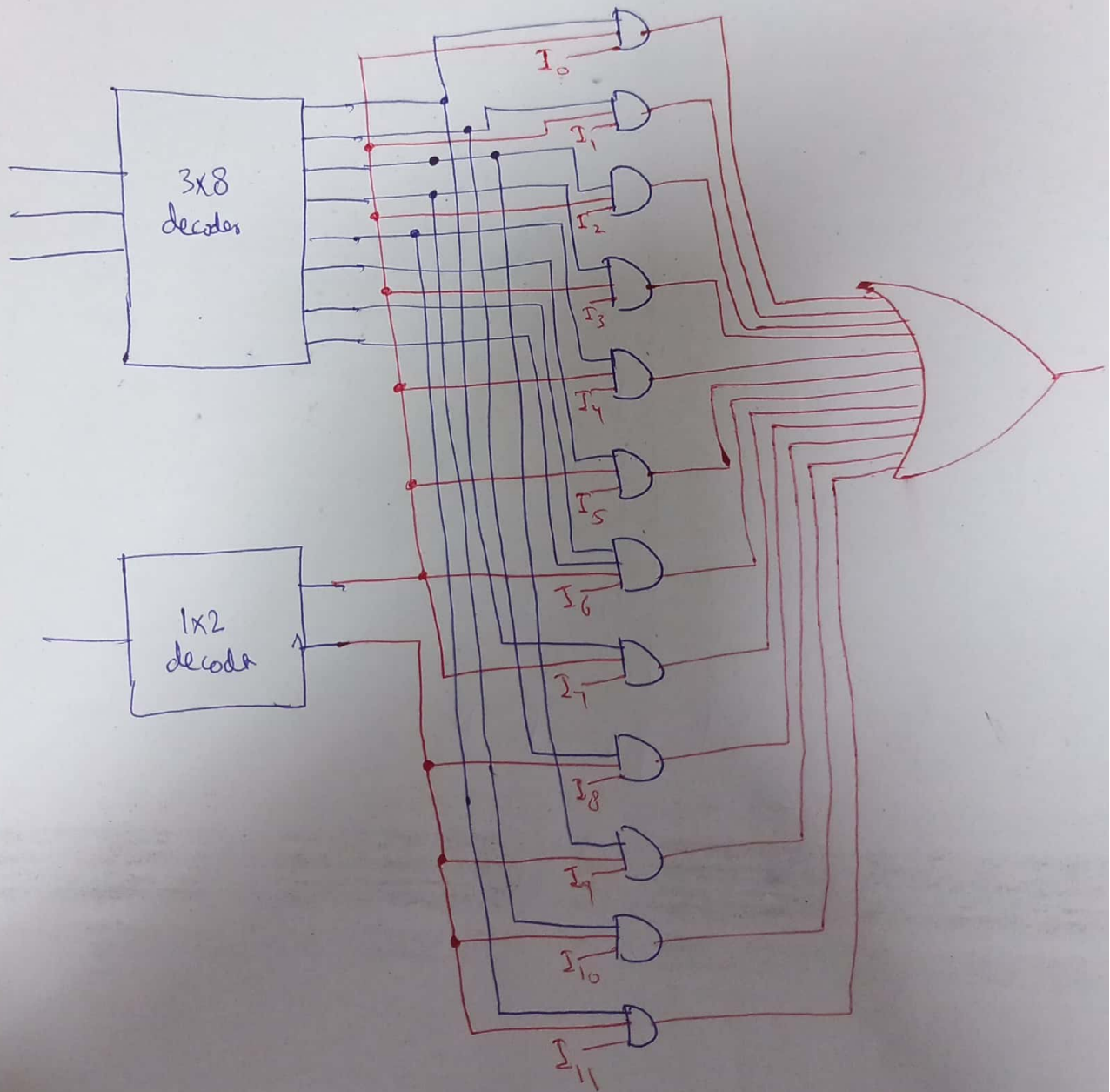

Question 02:

Implement the following Boolean function with an 8-to-1-line multiplexer and a single inverter with variable D as its input: [5M]

$$F(A, B, C, D) = \sum m(2, 4, 6, 9, 10, 11, 15)$$

A	B	C	D	F	
0	0	0	0	0	$F=0$
0	0	0	1	0	
0	0	1	0	1	$F=\bar{D}$
0	0	1	1	0	
0	1	0	0	1	$F=\bar{D}$
0	1	0	1	0	
0	1	1	0	1	$F=\bar{D}$
0	1	1	1	0	
1	0	0	0	0	$F=D$
1	0	0	1	1	
1	0	1	0	1	$F=1$
1	0	1	1	1	
1	1	0	0	0	$F=0$
1	1	0	1	0	
1	1	1	0	0	$F=D$
1	1	1	1	1	

