



Course:	Digital Logic Design Lab	Course Code:	EL-227
Program:	BS(Computer Science)	Total Marks:	45
Duration:	45 minutes	Page(s):	1
Paper Date:	20 March 2024		
Section:	E sec		
Exam:	MID LAB EXAM		


Note: 45 min inclusive of hardware and software.

Question 1:

Design a combinational circuit with a decoder to accept a 3-bit number and generate the output binary number equal to the square of the input number.

1. Give Truth table & Boolean expression for given problem (5)
2. Design it with 3 TO 8-line decoder (restriction is: Do it with NOR gates only).
 - Implement it on logic works (20)
 - Implement it on logic trainer (20)

$$A \times B$$

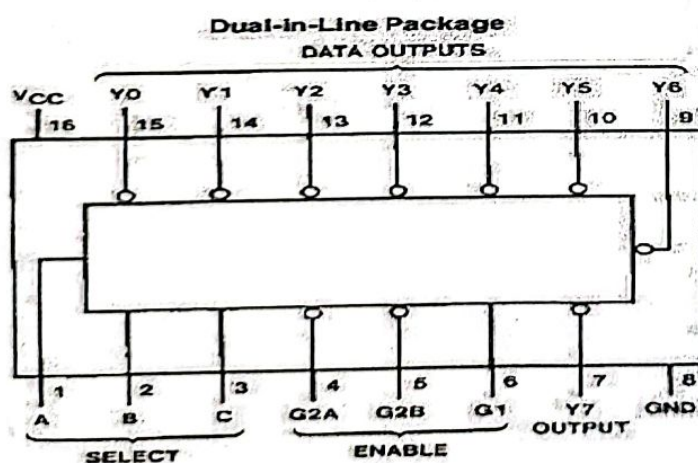

$$AND = AB = \overline{A+B} = AB$$

$$NAND = \overline{AB} = \overline{A+B}$$

$$\overline{\overline{A+B}} = \overline{\overline{A+B}} = A+B$$

(3,5)

Function Tables

DM74LS138

Inputs			Outputs									
Enable		Select										
G1	G2 (Note 1)	C B A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7		
X	H	X X X	H	H	H	H	H	H	H	H		
L	X	X X X	H	H	H	H	H	H	H	H		
H	L	L L L	L	H	H	H	H	H	H	H		
H	L	L L H	L	H	H	H	H	H	H	H		
H	L	L H L	L	H	H	H	H	H	H	H		
H	L	L H H	L	H	H	H	H	H	H	H		
H	L	H L L	L	H	H	H	L	H	H	H		
H	L	H L H	L	H	H	H	L	H	H	H		
H	L	H H L	L	H	H	H	L	H	L	H		
H	L	H H H	L	H	H	H	L	H	L	L		

H = HIGH Level
L = LOW Level
X = Don't Care

Note 1: G2 = G2A + G2B

$$7^2 = 49 = 66 \text{ bits.}$$

	I_2	I_1	I_0	O_5	O_4	O_3	O_2	O_1	O_0
$0^2=0$	0	0	0	0	0	0	0	0	0
$1^2=1$	0	0	1	0	0	0	0	0	1
$2^2=4$	0	1	0	0	0	0	1	0	0
$3^2=9$	0	1	1	0	0	1	0	0	1
$4^2=16$	1	0	0	0	1	0	0	0	0
$5^2=25$	1	0	1	0	1	0	0	0	0
$6^2=36$	1	1	0	1	0	0	1	0	0
$7^2=49$	1	1	1	1	1	0	0	0	1

NAND

2	25
2	12
6	0
3	0
1	1

$$= A\bar{B}(\bar{C}+C)$$

$$= A\bar{B} \checkmark$$

$$\bar{A}BC + A\bar{B}C$$

$$C(\bar{A}B + A\bar{B})$$

$$C(A \oplus B)$$

2	49
2	4
12	0
6	0
3	0
1	1

$$O_0 = I_0 = \sum m(1, 3, 5, 7)$$

$$O_1 = 0 = 0.$$

$$O_2 = \bar{I}_2 \bar{I}_1 \bar{I}_0 + \bar{I}_2 I_1 \bar{I}_0 \Rightarrow I_1 \bar{I}_0 = \sum m(2, 6)$$

$$O_3 = \bar{I}_2 \bar{I}_1 I_0 + \bar{I}_2 I_1 I_0 \Rightarrow I_0 (I_2 \oplus I_1) = \sum m(3, 5)$$

$$O_4 = \bar{I}_2 \bar{I}_1 + \bar{I}_2 I_0 = \sum m(4, 5, 7)$$

$$O_5 = \bar{I}_2 I_1 = \sum m(6, 7).$$

I_2	I_1	I_0	O_0	O_1	O_2	O_3	O_4	O_5
0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0