

# National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design Lab  
Program: BS (Computer Science)  
Duration: 20+20 mins  
Date: 05-03-18  
Section: D-2

Course Code: EL227  
Semester: Spring 2018  
Total Marks: 15  
Weight: 5%  
Pages: 2

## Quiz#1

### Question # 1

A	B	C	T <sub>1</sub>	T <sub>2</sub>
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

- a. Write Equation of Functions in SOP Form i-e as Sum of Min-terms Form (algebraic expression):

**T<sub>1</sub> (A, B, C) =**

---

**T<sub>2</sub> (A, B, C) =**

---

- b. Write Equation of Majority Function in POS Form i-e as Product of Maxterms Form (algebraic expression):

**T<sub>1</sub> (A, B, C) =**

---

**T<sub>2</sub> (A, B, C) =**

---

- c. Implement the complete circuit diagram (including T<sub>1</sub> and T<sub>2</sub>) of SOP form on LogicWorks and verify the outputs using timing diagrams.

**Note: Use 2-input Logic Gates only**

- d. Implement the complete circuit diagram (including T1 and T2) of POS form on LogicWorks and verify the outputs using timing diagrams.

**Note: Use 2-input Logic Gates only**

- e. Apply K-Map on equations of T1 (both SOP and POS) in order to minimize equations to the minimum number literals.

- f. Apply K-Map on equations of T2 (both SOP and POS) in order to minimize equations to the minimum number literals.