

# National University of Computer and Emerging Sciences, Lahore Campus



**Course:** Digital Logic Design  
**Program:** BS(Computer Science)  
**Duration:** 60 Minutes  
**Paper Date:** 1<sup>st</sup> Oct 2018  
**Section:** ALL  
**Exam:** Midterm-I

**Course Code:** EE227  
**Semester:** Fall 2018  
**Total Marks:** 60  
**Weight:** 15%  
**Page(s):** 5  
**Roll No.:**  
**Section:**

**Instruction/Notes:**

- Attempt all the questions on this answer booklet. You can use extra sheets for your scratch work but **they will not be collected and marked.**
- Make sure you write your roll # on EVERY sheet of the booklet.
- **Use of calculator is not allowed.**

## Question 1 [2+3+3+3+3 = 14 Marks] Short Questions

- 1's complement of a number N is 0110 1101, 2's Complement of N will be \_\_\_\_\_
- If  $F(X, Y, Z) = XY + X'Y'Z$  then  $F' =$  \_\_\_\_\_
- $F(A,B,C,D,E) = m_{23}$ . Algebraic expression for F will be  $F =$  \_\_\_\_\_
- $(10100)_2 + (30)_8 = (\text{_____})_{10}$
- Dual** of Boolean expression  $(X' + 0 + Z')$ .  $(X + Y' + Z)$  will be \_\_\_\_\_

**Question 2 [10 x 3 = 30 Marks]** A Boolean function is given as follows:

$$F(A,B,C,D) = \sum m(0,2,10,11)$$

$$d(A,B,C,D) = \sum m(1,3, 4, 6, 8, 9, 12, 14) \text{ [don't care]}$$

Use only **given KMaps** to optimize the function into:

**(i) Sum of Product (SOP) form**

A \ C	C			
	00	01	11	10
00				
01				
11				
10				

$F(A,B,C,D) =$  \_\_\_\_\_


**(ii) Product of Sum (POS) form**

A \ C	C			
	00	01	11	10
00				
01				
11				
10				

$F(A,B,C,D) =$  \_\_\_\_\_

**(iii) Implement the following optimized function with NAND gates ONLY. Complements of inputs are not directly available.**

$$F(A,B,C) = AB' + (A'B)C$$

 

**Question 3 [16 Marks]:** We want to design a combinational circuit that computes the function  $f(X) = 2X + 2$  for a 2-bit  $X$ :

**(a) How many bits do we need for output? (3 points)**

**(b) Draw the truth table for this function. (4 points)**

**(c) Write Simplified Boolean Expression(s) (3 points)**

**(d) Draw Circuit Diagram (6)**

## ROUGH SHEET