

National University of Computer and Emerging Sciences, Lahore Campus



Course: Digital Logic Design Lab
Program: BS(Computer Science)
Duration: 25
Date: 26-04-18
Section: D-2

Course Code: EL227
Semester: Spring 2018
Total Marks: 10
Weight: 5%
Pages: 2


Question # 1

Design a one-input, one-output serial 2's complemener. The circuit accepts a string of bits from the input and generates the 2's complement at the output.


- Construct the state table that consists of the present state, inputs and next state.
- Derive the next state equation/equations. Also show the simplification.
- Draw the logic diagram of sequential circuit.
- Draw the corresponding state diagram.

Solution:

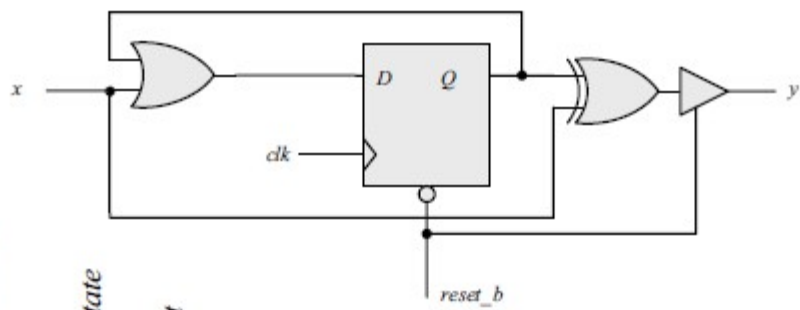The output is 0 for all 0 inputs until the first 1 occurs, at which time the output is 1. Thereafter, the output is the complement of the input. The state diagram has two states. In state 0: output = input; in state 1: output = input'.



Present state	Input	Next state	Output
A	x	A	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

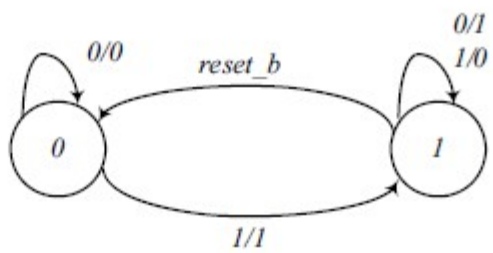

$$D_A = A + x$$

$$y = Ax' + A'x$$