

National University of Computer and Emerging Sciences, Lahore Campus



Course:	Digital Logic Design	Course Code:	EE-227
Program:	BS (Computer Science)	Semester:	Spring 2021
Duration:	10 Minutes	Total Marks:	10
Paper Date:	16-June-2021	Weight	3 %
Section:	C	Page(s):	2
Exam:	Quiz 2	Reg. No.	

Instruction/Notes: Calculators are strictly not allowed in all exams
Plagiarism will be dealt seriously causing an F in course

1. Design a combinational circuit that accepts a 3-bit number and generates a 6-bit binary number output equal to the square of the input number.

2. Implement the following Boolean function with an 8-to-1-line multiplexer and a single inverter with variable D as its input:

$$F(A, B, C, D) = \Sigma m(2, 4, 6, 9, 10, 11, 15)$$