

Lab # 8

Objectives:

- To learn the implementation of Boolean function using multiplexer
- To learn how to implement Multiplexers using decoders

2-to-4 line decoders:


74LS139 IC contains two fully independent 2-to-4 line decoders with active low enables. The function table and connection diagram for this IC are shown below:

Function Table:

Enable	Selection Inputs		Outputs			
G	B	A	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

H= Logic High, L= Logic Low, X= Don't Care

Connection Diagram:

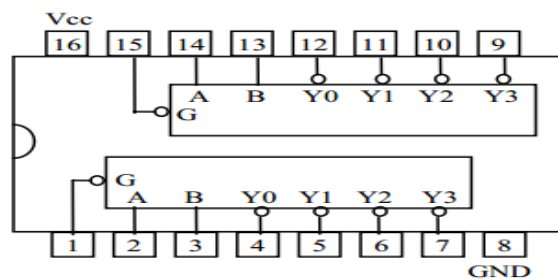

3-to-8 line decoders:

74LS138 IC contains 3-to-8 line decoder. The function table and connection diagram for this IC are shown below:


Function Tables
DM74LS138

Inputs		Select			Outputs							
Enable												
G1	G2 (Note 1)	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	H	H	H	H	H	H	H	H
H	L	L	L	H	L	H	H	H	H	H	H	H
H	L	L	H	L	H	L	H	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	L	H	H	H	H
H	L	H	L	H	H	H	H	H	L	H	H	H
H	L	H	H	L	H	H	H	H	H	L	H	H
H	L	H	H	H	H	H	H	H	H	H	L	H
H	L	L	H	H	H	H	H	H	H	H	H	L

H = HIGH Level
L = LOW Level
X = Don't Care

Note 1: $G2 = G2A + G2B$


Connection Diagram:

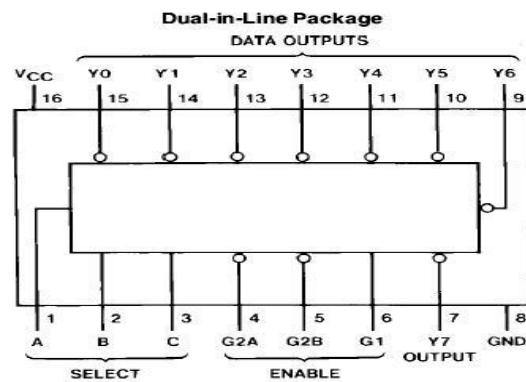

2x1 MUX:

74LS157 IC is a dual 4x1 MUX with active low enable.

74157/158

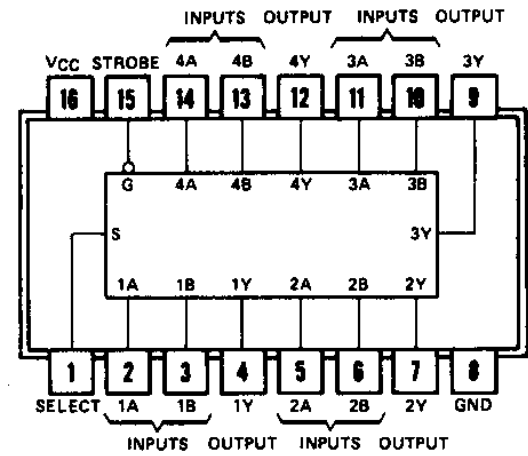

4x1 MUX:


74LS153 IC is a dual 4x1 MUX with active low enables. Two 4x1 MUXs with common selection pins but independent inputs and independent outputs is known as dual 4x1 MUX. The function table and connection diagram for this IC are shown below:

Function Table:

Strobe (Enable)	Selection Inputs		Data Inputs				Output
G	B	A	C0	C1	C2	C3	Y
H	X	X	X	X	X	X	L
L	L	L	L	X	X	X	L
L	L	L	H	X	X	X	H
L	L	H	X	L	X	X	L
L	L	H	X	H	X	X	H
L	H	L	X	X	L	X	L
L	H	L	X	X	H	X	H
L	H	H	X	X	X	L	L
L	H	H	X	X	X	H	H

H= Logic High, L= Logic Low, X= Don't Care

Connection Diagram:

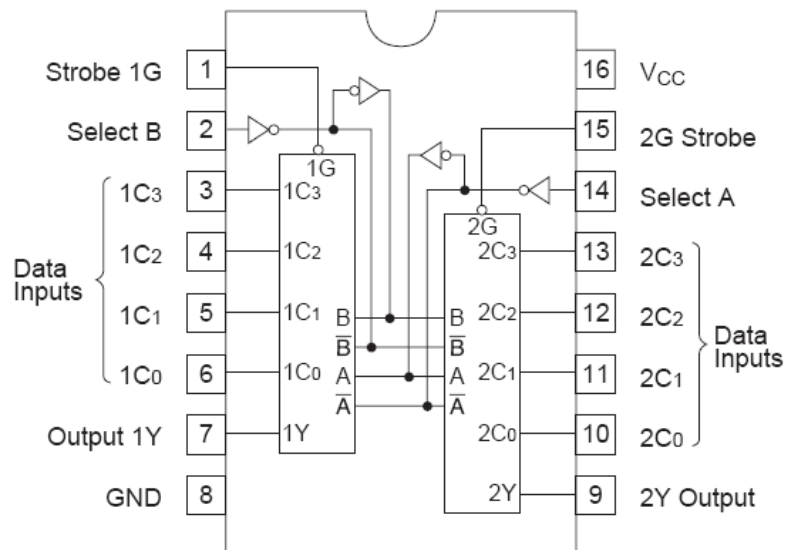

LAB TASKS

Question 1:

Implement 4x1 mux using one 2x4 decoder, four ANDs and one OR gate.

Question 2:

Implement the following function using 4x1 mux

$$F(X, Y, Z) = m_1 + m_2 + m_6 + m_7$$

Question 3:

Design a circuit that takes two 2-bit numbers and outputs their product.

POST LAB

Question 4:

Implement Dual 2x1 MUX Using 2x1 MUX(s) only