

National University of Computer and Emerging Sciences, Lahore Campus



Course:	Digital Logic Design Lab	Course Code:	EL227
Program:	BS(Computer Science)	Semester:	Spring 2018
Duration:	25	Total Marks:	10
Date	23-04-18	Weight	5%
Section:	B-2	Pages:	2

Question # 1

A sequential circuit with two D Flip-flops A and B, two inputs x and y, and one output z is specified by the following next-state and output equations.

$$A(t + 1) = x'y + xB$$

$$B(t + 1) = x'A + x'B$$

$$z = A$$

- Construct the state table that consists of the present state, inputs and next state.
- Draw the corresponding state diagram.
- Draw the logic diagram of sequential circuit.
- Briefly explain the working of this sequential circuit i-e what does it actually do?

Solution

Present state		Inputs		Next state		Output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

(c)

