

**National University of Computer and Emerging Sciences, Lahore Campus**



**Course:** Digital Logic Design  
**Program:** BS (Computer Science)  
**Duration:** 20 Minutes  
**Paper Date:** 22-June-2021  
**Section:** B  
**Exam:** Quiz 3

**Course Code:** EE-227  
**Semester:** Spring 2021  
**Total Marks:** 15  
**Weight:** 3 %  
**Page(s):** 2  
**Reg. No.**

**Instruction/Notes:** Calculators are strictly not allowed in all exams  
 Plagiarism will be dealt seriously causing an F in course

**1. For the following state table and state assignment, design a system using JK flip flops.**

Q	Q*		z	
	X=0	X=1	X=0	X=1
A	B	C	1	1
B	A	B	1	0
C	B	A	1	0

Q	Q <sub>1</sub>	Q <sub>2</sub>
A	1	1
B	1	0
C	0	1

2. A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:

$$D_A = XA + \bar{X}\bar{Y}, D_B = XB + \bar{X}A, Z = \bar{X}B$$

- (a) Draw the logic diagram of the circuit.
- (b) Derive the state table.
- (c) Derive the state diagram.
- (d) Is this a Mealy or a Moore machine?