

National University of Computer and Emerging Sciences, Lahore Campus



Course:	Digital Logic Design	Course Code:	EE227
Program:	BS(Computer Science)	Semester:	Fall 2018
Duration:	25 Minutes	Total Marks:	10
Quiz Date:	12-12-18	Weight:	
Section:	A	Page(s):	
Exam:	Quiz-5	Roll Number	

Show your working otherwise no credit will be given.

Q1. Design a counter with the following binary sequence 0,1,3,2,4,5,7. Use SR flipflops. (10marks)

National University of Computer and Emerging Sciences, Lahore Campus




Course:	Digital Logic Design	Course Code:	EE227
Program:	BS(Computer Science)	Semester:	Fall 2018
Duration:	25 Minutes	Total Marks:	20
Quiz Date:	29-11-18	Weight:	
Section:	A	Page(s):	
Exam:	Quiz-4	Roll Number	

Show your working otherwise no credit will be given.

Q1. The state equation for T-R flip-flop is $Q(t+1) = T'Q(t) + RT$. Construct a characteristic table for the flip flop. **[10 marks]**

 Q2 (a). What should be the logical value of clock Pulse (CP) at the time of enabling the flip-flop whose diagram is shown below? **[10 marks]**



CP = _____

(b) Fill the characteristic table of the above flip flop.

CP	A	B	Q(t+1)